
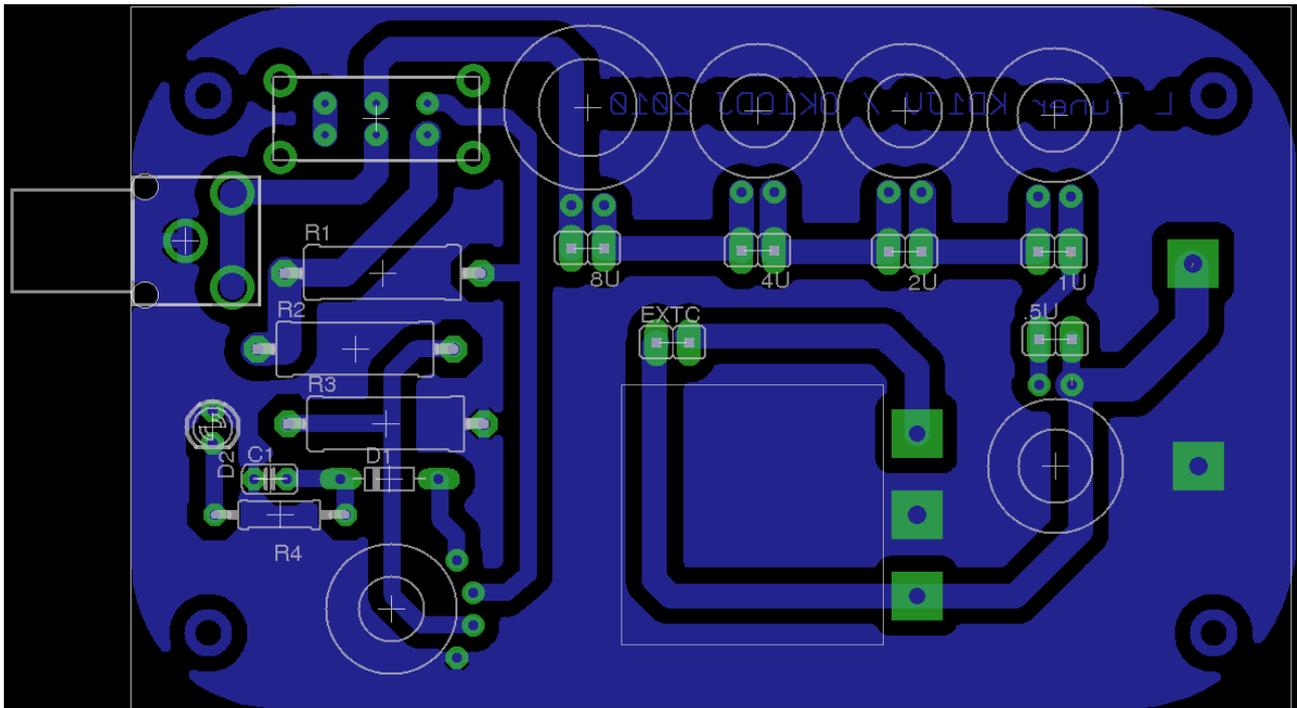


Altoids L Tuner

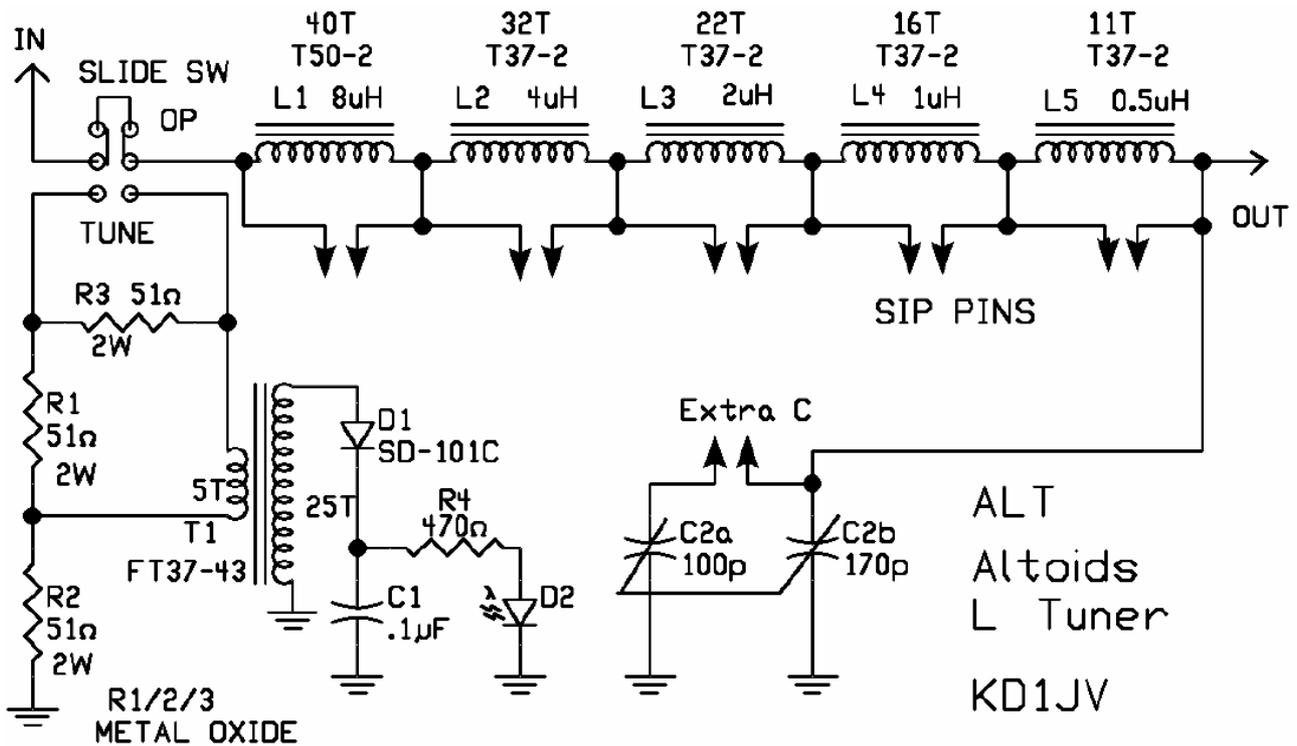Versatile L tuner for end feed wire antennas, fits in an Altoids tin. A compact and light weight system for use in the field by campers and backpackers.



- R1,R2,R3 - 51R / 2W
- R4 - 470R
- D1 - BAT43
- D2 - RED LED
- C1 - 100nF

Polyvaricon - you need to cut axis to half, because capacitor is too high for altoids case!!!

More info how to build tuner:

<http://kd1jv.qrpradio.com/alt/ALT.HTM>

<http://www.qrpkits.com/altoidslongwire.html>

<http://blog.ok1cdj.com/2010/11/altoids-l-tuner.html>